


| | | | |
|---|---|--|----------|
|  <p>ADAMAS UNIVERSITY PURSUE EXCELLENCE</p> | <p align="center">ADAMAS UNIVERSITY END-SEMESTER EXAMINATION : JANUARY 2021 (Academic Session: 2020 – 21)</p> | | |
| Name of the Program: (Example: B. Sc./BBA/MA/B.Tech.) | B.Tech | Semester: (I/III/ V/ VII/IX) | VIII |
| Paper Title : | Analog and Digital Electronics | Paper Code: | EEE42106 |
| Maximum Marks : | 40 | Time duration: | 3 hours |
| Total No of questions: | 8 | Total No of Pages: | 2 |
| (Any other information for the student may be mentioned here) | Any missing or misprinted information may be suitable assumed | | |

Answer all the Groups

Group A

Answer all the questions of the following

$5 \times 1 = 5$

1. a) Define open loop gain. [CO1]
- b) What is meant by radix (or base) of a number system? [CO2]
- c) Why hexadecimal code is widely used in digital systems? [CO3]
- d) What is meant by LSB and MSB? [CO2]
- e) What is flip-flop? [CO4]

GROUP –B

Answer *any three* of the following

$3 \times 5 = 15$

2. Convert SR flip flop into D flip flop and also draw excitation table [CO4]
3. A digital system has 4-bit input from 0000 to 1111. Design a logic circuit that produces high output when input is less than 1000. Use K-map technique. [CO4]
4. Prove $A + AB = A + B$ using Boolean algebra. [CO3]
5. Write short note on laws and axioms of Boolean algebra. [CO2]

GROUP –C

Answer *any two* of the following

$2 \times 10 = 20$

6. Explain full subtractor with proper circuit diagram and truth table [CO1]
 7. Construct a 16x1 multiplexer with two 8x1 and one 2x1 line multiplexer. [CO3]
 8. Simplify: $(A'+B+C).(A+B'+C)$. Draw simplified logic diagram. [CO4]
-