

 <p>ADAMAS UNIVERSITY PURSUE EXCELLENCE</p>	<p align="center">ADAMAS UNIVERSITY END-SEMESTER EXAMINATION : JANUARY 2021 (Academic Session: 2020 – 21)</p>		
Name of the Program: (Example: B. Sc./BBA/MA/B.Tech.)	B.Tech	Semester: (I/III/ V/ VII/IX)	VII
Paper Title :	Power Electronics	Paper Code:	EEE44103
Maximum Marks :	40	Time duration:	3 hours
Total No of questions:	8	Total No of Pages:	2
(Any other information for the student may be mentioned here)			

Answer all the Groups

Group A

Answer all the questions of the following

$5 \times 1 = 5$

1. a) What is latching current?
- b) What are the different thyristor protection techniques?
- c) Classify different types of inverter.
- d) What is the application of freewheeling diode in a rectifier circuit?
- e) Write the expression for average output voltage of a single-phase half wave rectifier with RL load.

GROUP –B

Answer *any three* of the following

$3 \times 5 = 15$

2. Discuss the V-I characteristics of thyristor.
3. Explain the working principle of on-off control method of an AC voltage controller.
4. With proper circuit, explain the working of a half bridge inverter circuit.
5. A single phase full bridge inverter has a resistive load of $R=5 \text{ Ohm}$ and the DC input voltage of 220 Volt. Compute:
 - a) RMS output voltage
 - b) Output power

GROUP –C

Answer *any two* of the following

$2 \times 10 = 20$

6. What is commutation of a thyristor? What are the different types of commutation?

Explain the operation of any two types of commutation. [2+2+6]

7. With proper circuit and voltage waveforms, explain the working of step up and step down chopper. [5+5]

8. A single phase full converter with RLE load. Given $V_s = 230$ Volt, 50Hz for $R = 2 \Omega$, $L = 10\text{mH}$, $E = 100\text{Volt}$. For firing angles of 30° Find output current and voltage in case the load current extinguishes at $\beta = 200^\circ$.
-