



ADAMAS UNIVERSITY

END SEMESTER EXAMINATION

(Academic Session: 2020 – 21)

Name of the Program:	BCA	Semester:	II
Paper Title:	Design of Logic Circuit	Paper Code:	CSE11405
Maximum Marks:	50	Time Duration:	3 Hrs
Total No. of Questions:	17	Total No of Pages:	2
(Any other information for the student may be mentioned here)	<ol style="list-style-type: none"> At top sheet, clearly mention Name, Univ. Roll No., Enrolment No., Paper Name & Code, Date of Exam. All parts of a Question should be answered consecutively. Each Answer should start from a fresh page. Assumptions made if any, should be stated clearly at the beginning of your answer. 		

Group A			
Answer All the Questions (5 x 1 = 5)			
1	Convert $(110110100011)_2$ to $()_{16}$.	Ap	CO1
2	What is the full form of CMOS?	R	CO2
3	Moore model uses only Entry Actions. True or False?	U	CO3
4	What is the full form of EEPROM?	R	CO4
5	ROMs are much faster than dedicated logic circuits. True or False?	U	CO4
Group B			
Answer All the Questions (5 x 2 = 10)			
6 a)	Using the Karnaugh map, obtain the Boolean expression for $F(A, B, C, D) = \sum_m(0,4,7,9,13,15) + \sum_d(3,5)$	Ap	CO1
(OR)			
6 b)	Draw the logic diagram and derive the Boolean expression of a half-subtractor.	U	CO1
7 a)	Define Fan-in and Fan-out.	R	CO2
(OR)			
7 b)	What is the utility of CMOS?	R	CO2
8 a)	Define Mealy Machines.	R	CO3
(OR)			
8 b)	Describe the universal logic gates.	R	CO3
9 a)	Describe the different laws of Boolean algebra.	R	CO1
(OR)			
9 b)	Draw the logic circuit and truth table of a 2×4 decoder.	Ap	CO1
10 a)	Give the logic diagram and state transition table of a T F/F.	U	CO4
(OR)			
10 b)	Give the logic diagram and state transition table of an S-R F/F.	U	CO4
Group C			
Answer All the Questions (7 x 5 = 35)			
11 a)	Using the Karnaugh map, minimise the following Boolean expression: $F(A, B, C, D) = \sum_m(1,2,3,8,9,10,11,14) + \sum_d(7, 15)$ and draw the logic circuit for the minimized expression	Ap	CO1
(OR)			
11 b)	Draw the logic circuit diagram of a 2:1 MUX and by using it, design a 4:1 MUX.	Ap	CO1

12 a)	Briefly describe the family of logic gates	R	CO2
(OR)			
12 b)	Write short note on CMOS.	R	CO2
13 a)	Explain the functionality of Moore machine.	U	CO3
(OR)			
13 b)	Differentiate between Moore & Mealy machine.	R	CO3
14 a)	Write short note on ROM	U	CO4
(OR)			
14 b)	Explain how ROM is used as a PLD.	Ap	CO4
15 a)	Explain Full Adder with logic circuit diagram, truth table and Boolean expression	U	CO1
(OR)			
15 b)	Explain XOR and XNOR with logic diagrams and truth tables.	U	CO1
16 a)	Realize $f(A, B, C) = (a + bc)(b + c'a)$ using only NOR gates.	Ap	CO1
(OR)			
16 b)	Differentiate between K-map and Quine-McCluskey method	R	CO1
17 a)	Describe the different shift registers.	U	CO4
(OR)			
17 b)	Differentiate between S-R latch and S-R Flip-Flop	U	CO4

Note: The Sample prepared by assuming 5 COs in a course, considering one CO for one Module.

- i) If the COs are higher in numbers that can be managed by equating sub-divisional questions
- ii) If the COs are lower in numbers, the questions can be increased by equating the number of COs