 <p><b>ADAMAS UNIVERSITY</b> PURSUE EXCELLENCE</p>	<p align="center"><b>ADAMAS UNIVERSITY</b>  <b>END-SEMESTER EXAMINATION: JANUARY 2021</b>          (Academic Session: 2020 – 21)</p>		
<b>Name of the Program:</b> (Example: B. Sc./BBA/MA/B.Tech.)	B. Tech ECE	<b>Semester:</b> (I/III/ V/ VII/IX)	III
<b>Paper Title :</b>	Analog Electronic Circuits	<b>Paper Code:</b>	EEC42103
<b>Maximum Marks:</b>	40	<b>Time duration:</b>	3 hours
<b>Total No of questions:</b>	<b>08</b>	<b>Total No of Pages:</b>	02
(Any other information for the student may be mentioned here)			

**Answer all the Groups**

**Group A**

Answer all the questions of the following

$5 \times 1 = 5$

1.

- a) What is piezoelectric crystal?
- b) What is operating point?
- c) What is TUF of a rectifier?
- d) Draw the small signal model of a FET.
- e) A transistor having  $\alpha = 0.98$  and  $V_{BE} = 0.7V$ , is shown in the figure 1. Find out the value of the collector current.

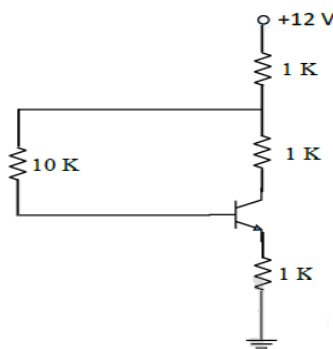


Figure 1

**GROUP –B**

Answer any three of the following

$3 \times 5 = 15$

2. What is negative feedback? Write the effects of negative feedback on an amplifier. [1+4=5]

3. What is output offset voltage? Draw the Astable multivibrator circuit using 555 timer and explain it. [1+4=5]
4. What is peak inverse voltage (PIV)? Draw the full wave bridge rectifier circuit and explain it with input and output wave form. [1+4=5]
5. Draw small signal equivalent circuit of a FET and define transconductance, drain resistance and amplification factor. [1+4=5]

### GROUP –C

Answer *any two* of the following

$2 \times 10 = 20$

6. What is thermal runaway? A Ge transistor with  $\beta=49$  has the self-biasing arrangements. If  $V_{cc}=12V$ ,  $R_1=2K\Omega$ ,  $R_2=500\Omega$ ,  $R_L=2K\Omega$  and  $V_{BE}=0.2V$ , find the stability factors  $S$ ,  $S'$ . What is Zener breakdown? Explain clipper circuit with diagram. [2+4+2+2=10]
7. What is positive feedback? Explain effect of negative feedback on bandwidth of an amplifier in details. Explain Hartley oscillator with proper circuit diagram. [1+5+4=10]
8. What is virtual ground? Draw the circuit diagram of differential amplifier and find out the input output relation. Calculate the value of output voltage for a non-inverting amplifier if  $R_f=10K$ ,  $R=1.5K$  and amplitude of input signal is 5 mv (p-p). [2+5+3=10]

---