



ADAMAS UNIVERSITY

END SEMESTER EXAMINATION

(Academic Session: 2020 – 21)

Name of the Program:	BCA	Semester:	II
Paper Title:	DIGITAL ELECTRONICS	Paper Code:	ECE11501
Maximum Marks:	50	Time Duration:	3 Hrs
Total No. of Questions:	17	Total No of Pages:	02
(Any other information for the student may be mentioned here)		1. At top sheet, clearly mention Name, Univ. Roll No., Enrolment No., Paper Name & Code, Date of Exam. 2. All parts of a Question should be answered consecutively. Each Answer should start from a fresh page. 3. Assumptions made if any, should be stated clearly at the beginning of your answer.	

Group A			
Answer All the Questions (5 x 1 = 5)			
1	How many two-inputs AND & OR gates are required to realize $Y=CD+EF+G$ a) 2,2 b) 2,3. c) 3,3 d) none of these.	R	CO1
2	Solve the Boolean expression $\overline{A}BC + \overline{A}BC$	AP	CO2
3	In a 1:8 de-multiplexer, the number of select lines are a) 4 b) 1 c) 3 d) 2	U	CO3
4	What are the differences between ROM & RAM?	R	CO4
5	The register that is loaded with parallel data with the stored data being available at the output serially one bit at a time is the type a) SISO b) SIPO c) PISO d) PIPO	R	CO5
Group B			
Answer All the Questions (5 x 2 = 10)			
6 a)	Design and implement EX-OR gate using NOR gate.	C	CO2
(OR)			
6 b)	On subtracting $(001100)_2$ from $(101001)_2$ using 2's complements, construct the value?	AP	CO1
7 a)	Simplify and draw the logic diagram for the given expression $F = \overline{A}BC + \overline{A}BC + \overline{A}BC + \overline{A}BC + \overline{A}BC$	AN	CO2
(OR)			
7 b)	Construct 16:1 MUX by using 4:1 MUX only.	AP	CO3
8 a)	Simplify the expression $Y = \prod (0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$ using the K-map method	AN	CO3
(OR)			
8 b)	Compare between PROM, PLA & PAL.	E	CO4
9 a)	Determine the initial clock frequency of 4-bit ripple counter, if the period of waveform at the last flip-flop is 64 microseconds.	E	CO5
(OR)			
9 b)	Explain propagation delay in ripple counter.	U	CO5

10 a)	Determine the binary numbers represented by the following decimal numbers. (i) 25.5 (ii) 10.625	E	CO1
(OR)			
10 b)	Define Associative property of Boolean algebra.	R	CO2
Group C Answer All the Questions (7 x 5 = 35)			
11 a)	i) Compare between Weighted Binary Codes and Non-Weighted Binary Codes [2] ii) Construct the decimal number 82.67 to its binary, hexadecimal and octal equivalents. [3]	AN, AP	CO1
(OR)			
11 b)	Draw the logic diagram of a full subtractor and explain its working with the help of a truth table.	U	CO2
12 a)	Simplify the expression using Karnaugh map $Y = \sum_m (0, 1, 4, 5, 8, 9, 12, 13, 14)$, $d (2, 3, 6)$ and draw the equivalent circuit using logic gates.	AN	CO3
(OR)			
12 b)	Design and implement the circuit using 4-bit EXCESS-3 to BCD converter and simplify the expression using Karnaugh map.	C	CO2
13 a)	What is an Encoder? Draw the logic circuit of a 8-line to 3-line Encoder and explain its working.	R	CO3
(OR)			
13 b)	Explain the operation of master slave J-K flip flop and show how the race around condition is eliminated in it.	U	CO3
14 a)	Design 4x1 MUX using Boolean function $F(A,B,C,D) = \sum_m (1, 4, 5, 7, 9, 12, 13)$.	C	CO3
(OR)			
14 b)	Write the different conditions to check for determining the type of Decoder, number of AND gates and OR gates for realization of Boolean expression using PLDs. Realize the following set of logical expressions using ROM, PLA and PAL. $Y_1 = AC + \bar{A}B$ $Y_2 = ABC + AB\bar{C} + \bar{A}BC$ $Y_3 = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C$	E	CO4
15 a)	Design a 4-bit asynchronous up counter using negative edge triggered and show the timing diagram.	C	CO5
(OR)			
15 b)	Design PISO shift register and explain the data movement technique.	C, U	CO5
16 a)	i) Write down the differences between synchronous and asynchronous counters. ii) Design Mod-6 Synchronous up counter using T flip flop.	R, C	CO5
(OR)			
16 b)	Compare between static and dynamic RAM. Draw the circuits of one cell of each and explain its working.	E	CO4
17 a)	Construct the D FF from JK FF using its corresponding characteristics & excitation table.	AP	CO3
(OR)			
17 b)	Change the S-R FF to D FF using its corresponding characteristics & excitation table.	C	CO3